

Multiplexer:

if s :

return x_2

else:

return x_1




n (min terms) $\approx n$ (max terms)

$$f = \sum m(2, 3, 5, 7) = !s x_1 + s x_2$$


$$= \prod M(0, 1, 4, 6) = (s + x_1)(!s + x_2)$$

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1



2-to-1 multiplexer:

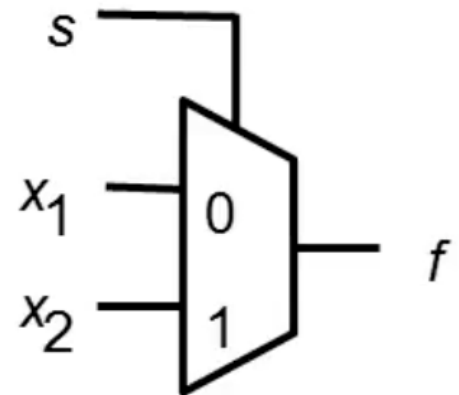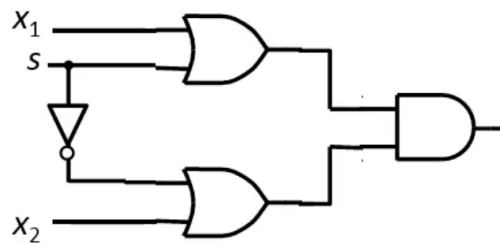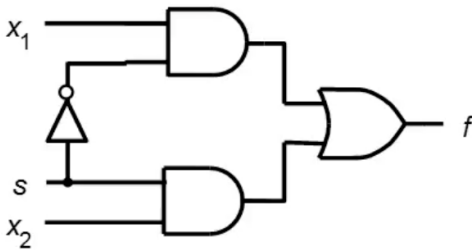

4-to-1 (s_1, s_0)

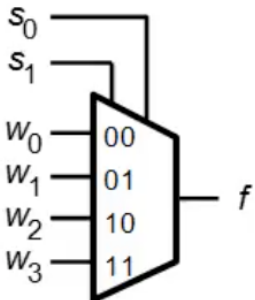

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

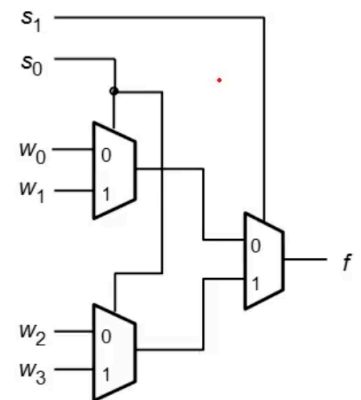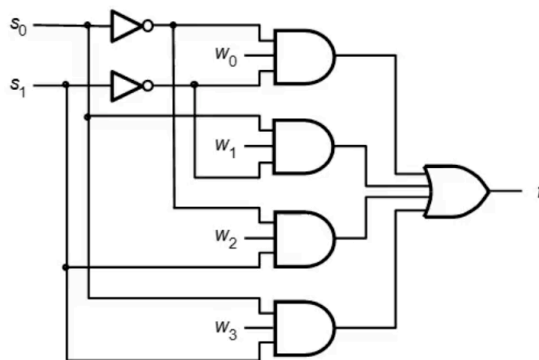

$n = 2^k$ for k in \mathbb{N} , n -to-1 multiplexer has:


n inputs

1 output

k selection control inputs

$$\begin{cases} f = x_1 & \text{if } s = 0 \\ f = x_2 & \text{if } s = 1 \end{cases}$$

s	$f(s, x_1, x_2)$
0	x_1
1	x_2

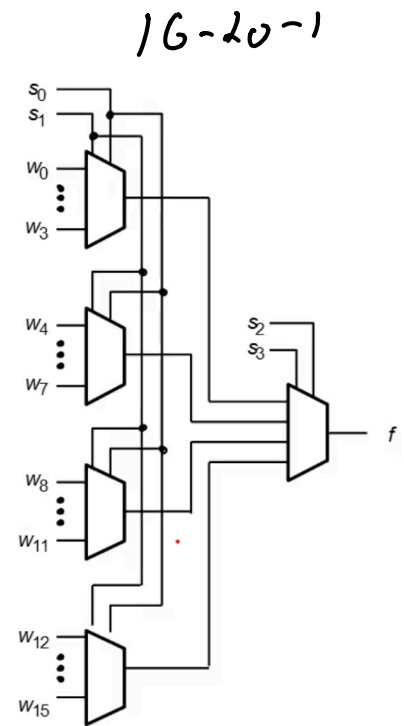


Crossbar switch

If $s = 0$, crossbar connects:


- x_1 to y_1
- x_2 to y_2

If $s = 1$, crossbar connects:


- x_1 to y_2
- x_2 to y_1

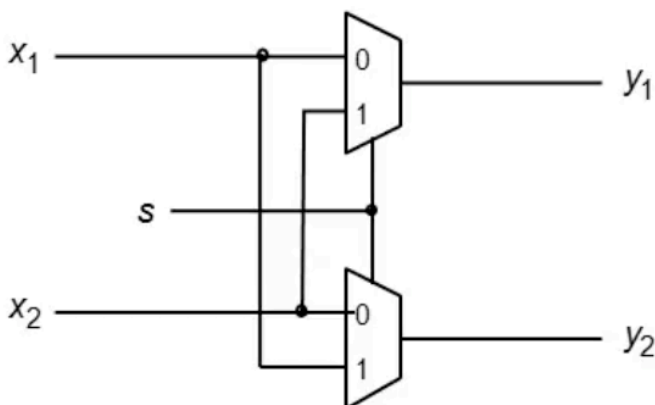


(b) Implementation using multiplexers

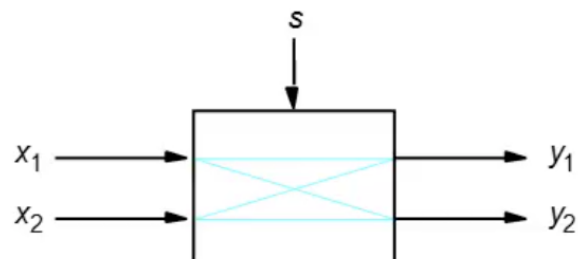


(a) A 2x2 crossbar switch

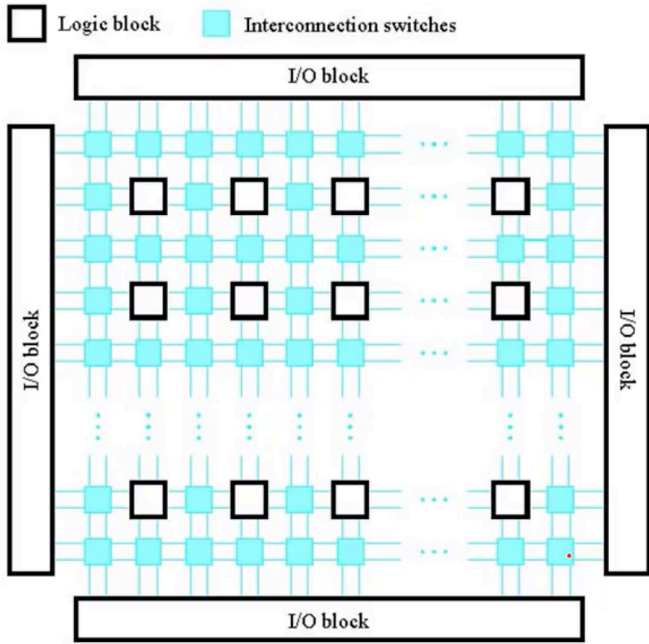

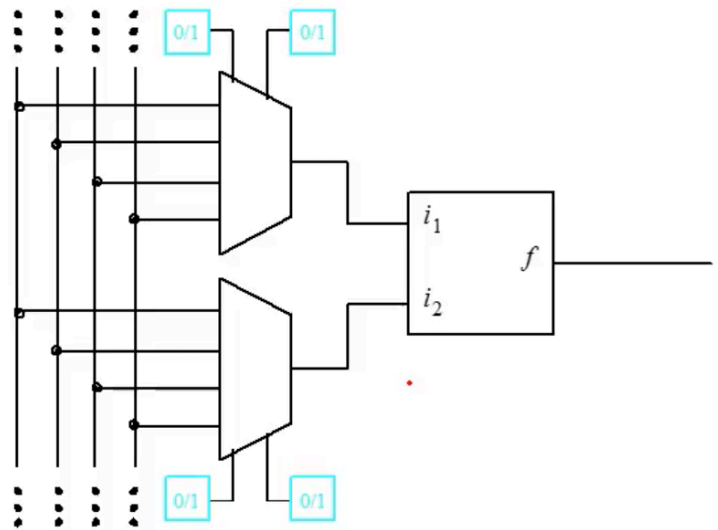The interconnection between logic blocks can be implemented using 4-to-1 multiplexers.



Can implement any logic gate:

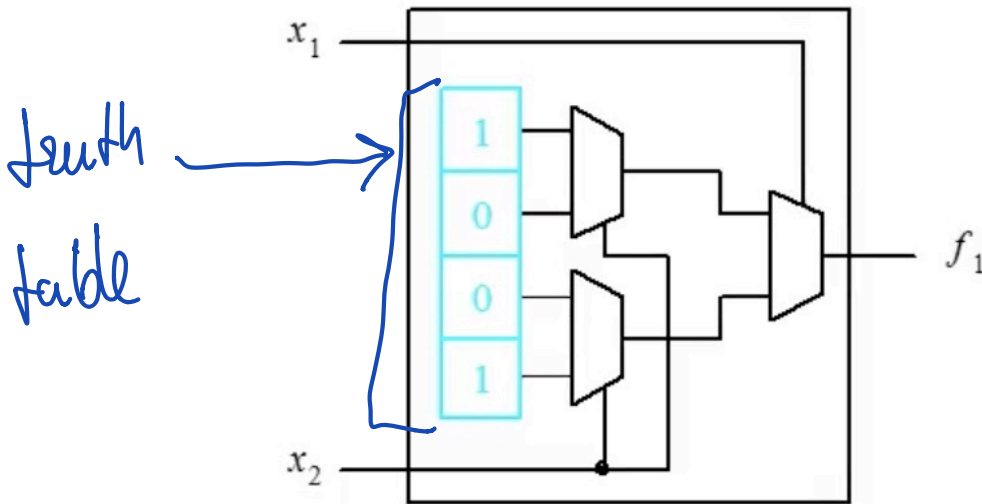

lookup table (LUT)

$$f(w_1, \dots, w_n) = \underbrace{w_1 f(0, w_2, \dots, w_n) + w_1 f(1, w_2, \dots, w_n)}_{\text{co factor of with respect to } w_1, \dots, \text{ to } w}$$

if term of f has $\neg w_1 \rightarrow$ goes to $\neg w_1 (\dots)$
 $w_1 \rightarrow w_1 (\dots)$
doesn't have $w_1 \rightarrow$ goes to both

factoring out all of the terms leads to a canonical SOP expression.

