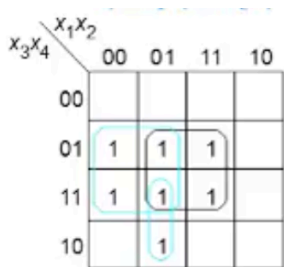


Don't care condition - that never occurs


Incompletely specified function - has Don't care conditions

Don't cares are represented as:  $d$  in K-maps  
 $D$  in SOP and POS


$$f = \sum m(1) + D(2, 3) = \prod M(0) + D(2, 3)$$



(a) Optimal realization of  $f_3$

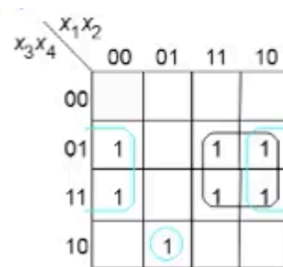


(b) Optimal realization of  $f_4$

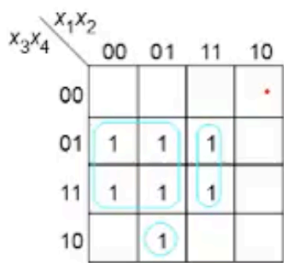

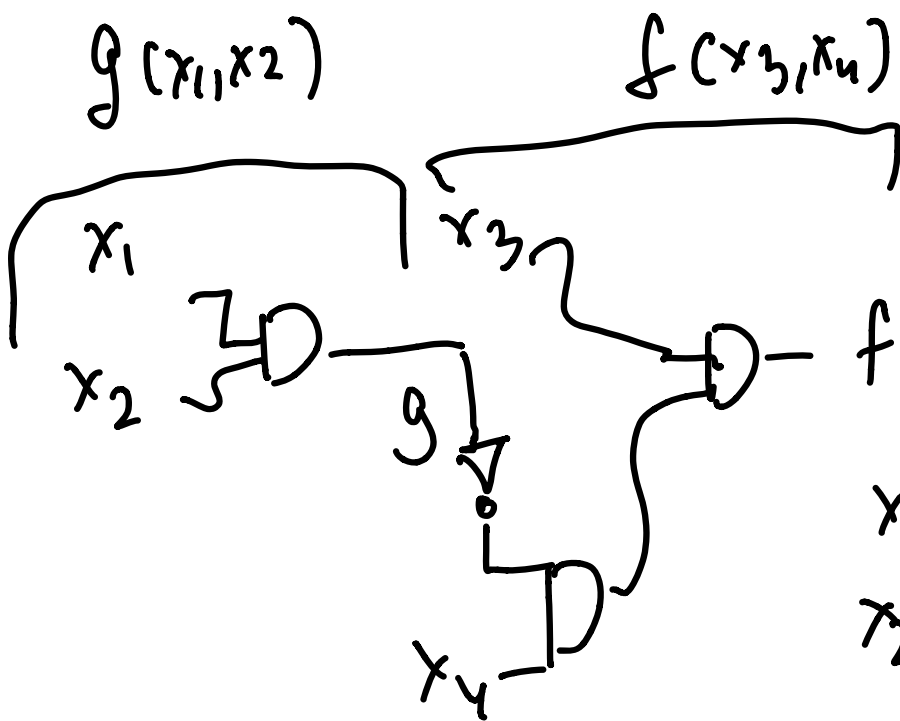
(c) Optimal realization of  $f_3$  and  $f_4$  together

Fan-in problem occurs when the second level is large  
(1st is And for SOP, 2nd is OR)

Multilevel logic expression - solves fan-in  
(cheaper, but slower)



(block diagram)

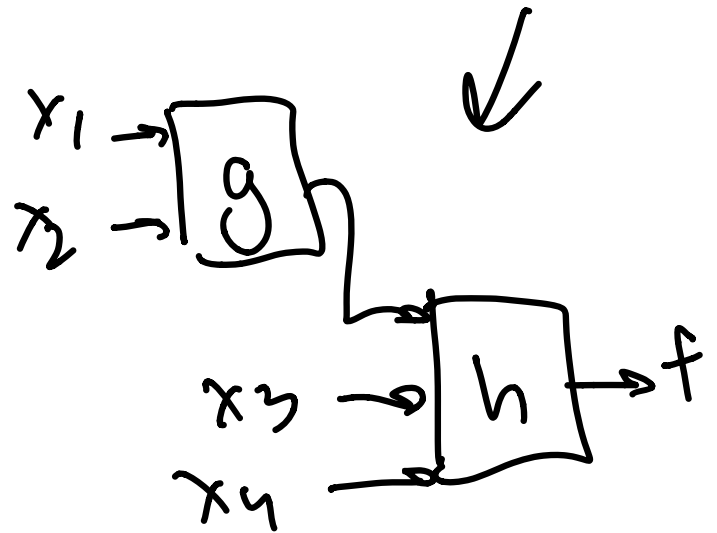

$x_3x_4$	$x_1x_2$			
	00	01	11	10
00	1			
01		1	1	1
11				
10	1			

$$x_5 = 0$$

$x_3x_4$	$x_1x_2$			
	00	01	11	10
00				
01	1	1	1	1
11				
10	1	1	1	1

$$x_5 = 1$$

$$f = gk + \neg g \neg k$$

$$g = x_1 + x_2 + x_5$$

$$k = \neg x_3 x_4 + x_3 \neg x_4$$

$$g(a) = a \quad f(a, b) = gb \quad (\text{disjoint composition})$$

$$f(a, b) = gb + a \quad (\text{non-disjoint composition})$$

(cause  $a$  is used

locally and globally)