

$$\neg x_1 \neg x_2 + \neg x_1 x_2 + x_1 x_2$$

$$\neg x_1 (\neg x_2 + x_2) \quad x_2 + \neg x_1 \neg x_2$$

$$\neg x_1 + x_1 x_2 \quad x_2 + (\neg x_1 + x_2)$$

$$\neg x_1 (1 + x_2) \quad x_1 + x_2$$

$$\neg x_1 + x_2$$

$$\neg x_1 \neg x_2 + \neg x_1 x_2 + x_1 x_2$$

$$\neg x_1 + x_1 x_2$$

$$\neg x_1 + x_2$$

| Π | x_1 | x_2 | x_3 | Min term |
|-------|-------|-------|-------|---------------------------------------|
| 0 | 0 | 0 | 0 | $m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$ |
| 1 | 0 | 0 | 1 | $m_1 = \bar{x}_1 \bar{x}_2 x_3$ |
| 2 | 0 | 1 | 0 | $m_2 = \bar{x}_1 x_2 \bar{x}_3$ |
| 3 | 0 | 1 | 1 | $m_3 = \bar{x}_1 x_2 x_3$ |
| 4 | 1 | 0 | 0 | $m_4 = x_1 \bar{x}_2 \bar{x}_3$ |
| 5 | 1 | 0 | 1 | $m_5 = x_1 \bar{x}_2 x_3$ |
| 6 | 1 | 1 | 0 | $m_6 = x_1 x_2 \bar{x}_3$ |
| 7 | 1 | 1 | 1 | $m_7 = x_1 x_2 x_3$ |

$$b \quad 1 \quad 1 \quad 0 \quad 6 = x_1 x_2 x_3$$

$$z \quad 1 \quad 1 \quad 1 \quad m_7 = x_1 x_2 x_3$$


$$\begin{array}{ccc|c} 0 & 0 & 1 & !x_1, !x_2 \cdot 1 \\ 0 & 1 & 1 & !x_1, x_2 \cdot 1 \\ 1 & 0 & 0 & x_1, !x_2 \cdot 0 \\ 1 & 1 & 1 & x_1, x_2 \cdot 1 \end{array}$$

$$!x_1, !x_2 \vee !x_1, x_2 \vee x_1, !x_2 \vee x_1, x_2$$


a) Canonical sum of - products
(regular solution)

b) Minimal-cost realization
(most efficient solution)

Cost = #gates + #inputs

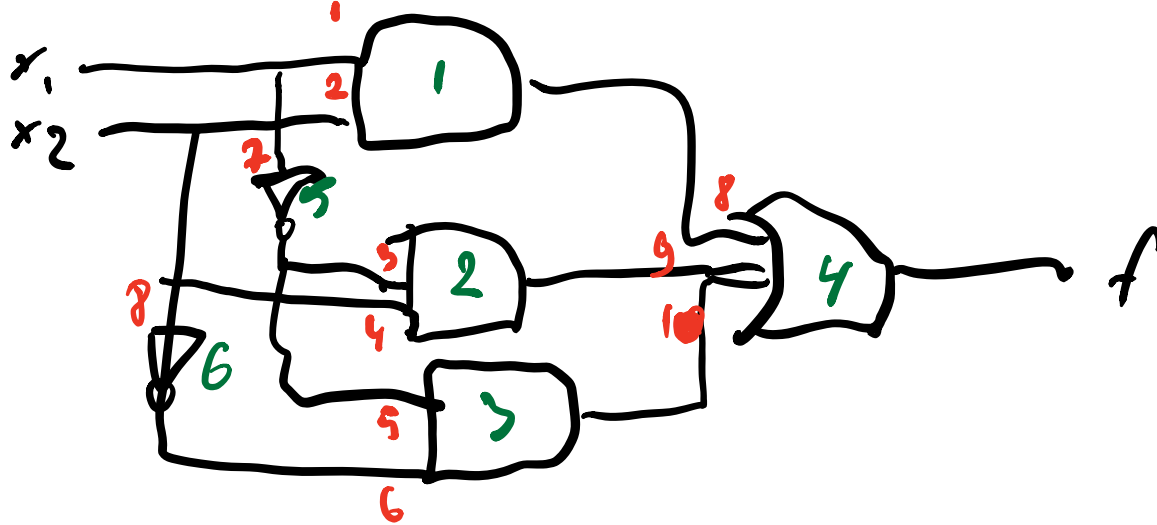

$$6 + 11 = 17$$

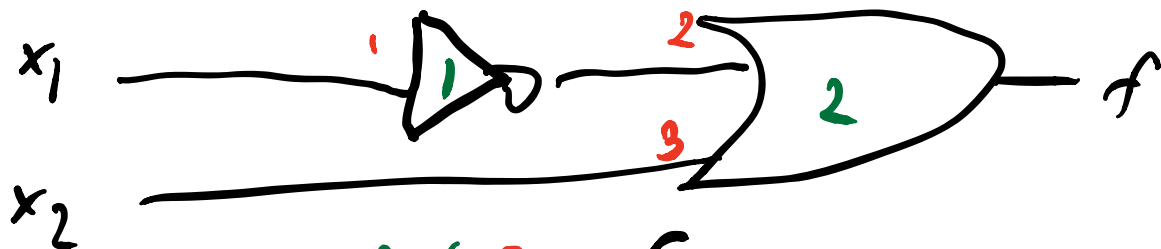

$$2 + 3 = 5$$

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6) =$$

$$= \sum m(1, 4, 5, 6)$$

rows that are 1

= Canonical SOP expression
Sum-of-product,

m - **minterm** $0 = \bar{x}$ $1 = x$ (all = 1)
 M - **Maxterm** $0 = x$ $1 = \bar{x}$ (all = 0)

Product-of-sums (POS) - inverse of SOP


$$(x+y)(!x+y)(!x-!y)$$

Σ - sum


Π - product

$$\begin{aligned}
 f(x_1, x_2, x_3) &= \Pi(M_0, M_2, M_3, M_7) = \\
 &= \Pi M(0, 2, 3, 7)
 \end{aligned}$$

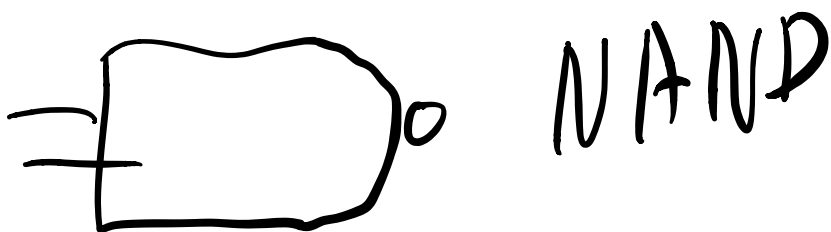in N $f = \Pi M(\epsilon) = \Sigma m(\text{not } \epsilon)$




NAND

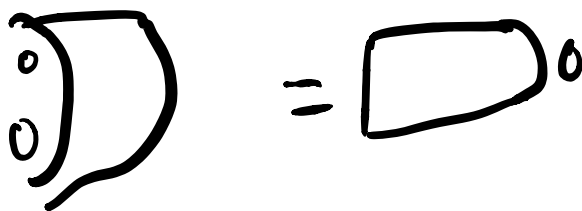


Invert outputs of AND
Invert inputs of OR
Use 1stth to convert OR to NAND
Use NAND for inversions

| x | y | or | and | nand | nor |
|---|---|----|-----|------|-----|
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 |

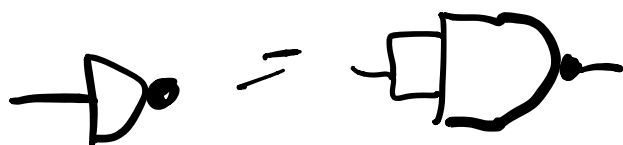

NOR

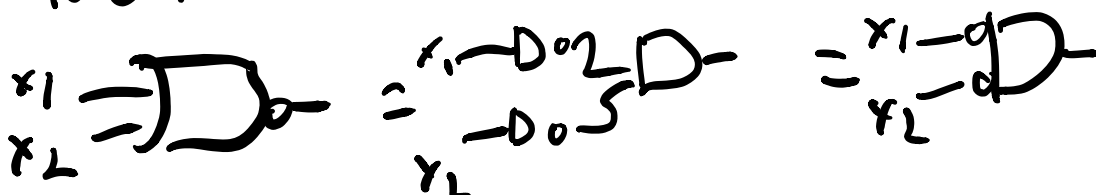

$$1 \quad (x_1 + x_2) = \bar{x}_1 \bar{x}_2$$

invert outputs of OR

invert inputs of AND

Use 15th to convert AND to NOR

Use NOR for inversions