 


One-hot encoded output - only 1 of the outputs is 1 at a time
 For n decoder inputs, you get 2^n decoder outputs


2-to-4 decoder

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table




(b) Graphical symbol

 


(c) Logic circuit


3-to-8 decoder

 


4-to-16 decoder

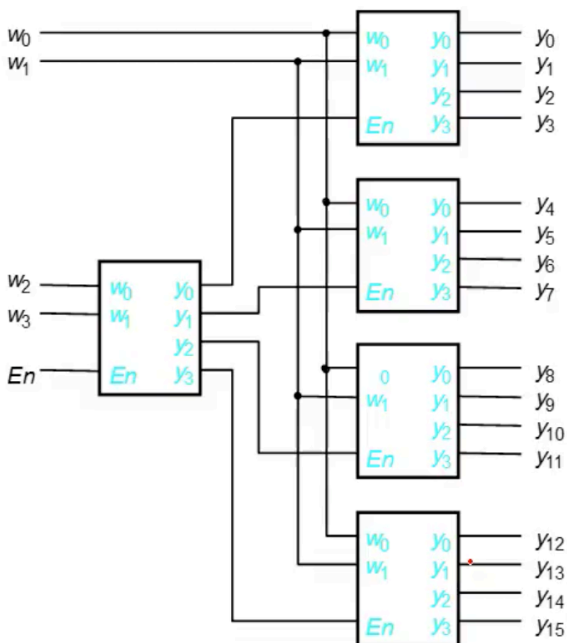


multiplexer using a decoder

 

 
Demultiplexer - opposite of the multiplexer



Memory bus using decoder

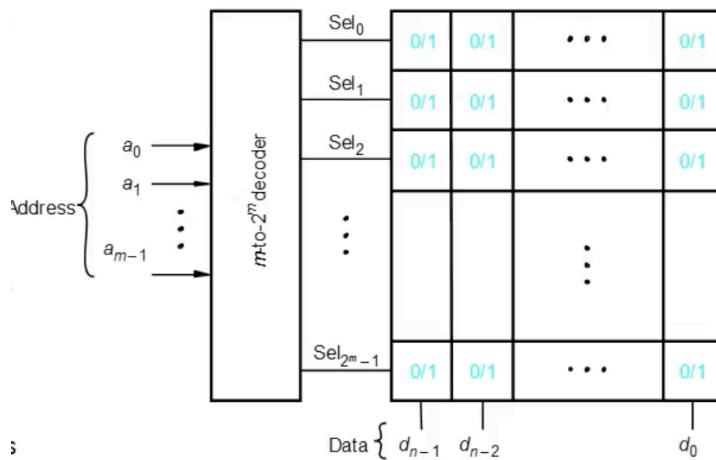

Encoders

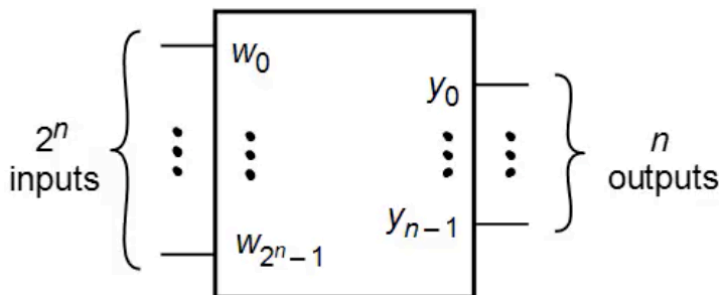

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Can build the circuit

by inspection:

$$y_0 = w_1 + w_3$$

$$y_1 = w_2 + w_3$$

Priority Encoder


w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

Comparator

$$\begin{aligned}
 AeqB &= i_3 \cdot i_2 \cdot i_1 \cdot i_0 \\
 AgtB &= a_3!b_3 + i_3a_2!b_2 + i_3i_2a_1!b_1 + i_3i_2i_1a_0!b_0 \\
 AltB &= !(AeqB + AgtB) \\
 AgeB &= !AltB \text{ or } AgeB = AgtB + AeqB \\
 AleB &= !AgtB \text{ or } AleB = AltB + AeqB
 \end{aligned}$$

where $i_n = !(a_n \oplus b_n)$ // not the same

Signed Comparator

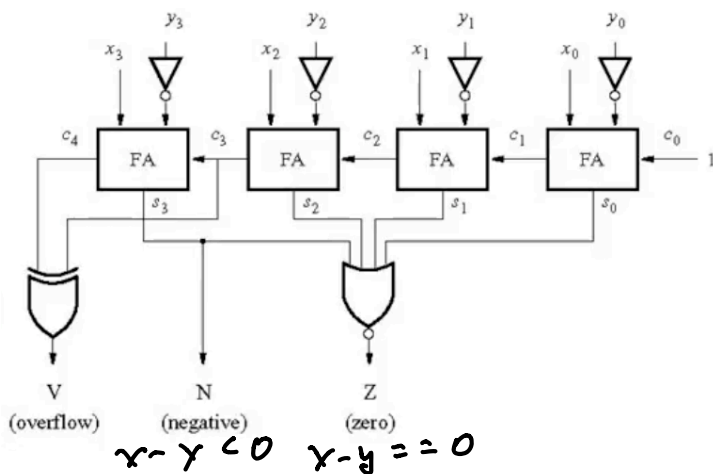

Thus with:

$$XeqY = Z$$

$$XltY = N \oplus V$$

We can derive the rest as follows:

$$XleY = XeqY + XltY = Z + (N \oplus V)$$

$$XgtY = !XleY = !(Z + (N \oplus V))$$

$$XgeY = !XltY = !(N \oplus V)$$

What about $X < Y$?


- If X and Y have the same sign:
 - There will be no overflow ($V = 0$)
 - And $X - Y$, will be negative ($N = 1$)
- If X is negative & Y is positive or zero:
 - $X - Y$ will be negative ($N = 1$), if there is no overflow ($V = 0$)
 - But the result will be positive ($N = 0$), if there is overflow ($V = 1$).
- If X is positive & Y is negative or zero:
 - $X > Y$, so we don't have to worry about this case
- $X \text{lt} Y = N \oplus V$

Combinational logic - outputs depend on inputs only
Sequential Logic - may depend on external too
(have memory)

Memory Elements

• Basic SR latch (Set-Reset)

S	R	Q_a	Q_b
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

 

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

